

• Main Idea of Task : (REST DAYS)

We need to reset counters of Days according to number that displays in Months 7 segment.

So we first have to determine months that we rest at 31 or 30 or 28 days.

 $1,3,5,7,8,10,12 \rightarrow 31 \text{ Days}$

4,6,9,11 → 30 Days


 $2 \rightarrow 28 \text{ Days}$

Month	Num of days
1	31
2	28
3	31
4	30
5	31
6	30
7	31
8	31
9	30
10	31
11	30
12	31

Element used and its usage

1- 74154 Decoder

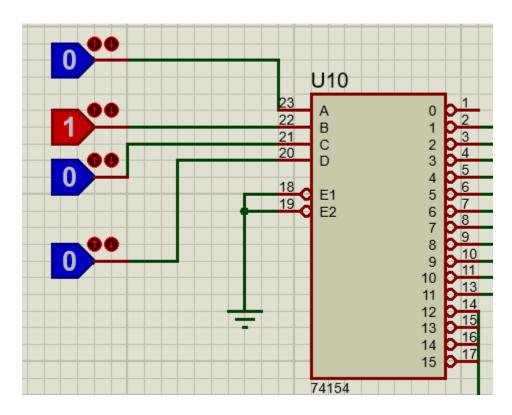
It takes input as binary and converts it to decimal active low



2- 2 Nand gates

Because of active low of Decoder we use NanD instead of OR


NAND GATE

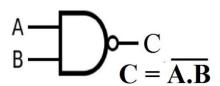


INPUT OUTPUT A В A NAND B 0 0 1 1 0 1 1 0 1 1 1 0

Truth Table

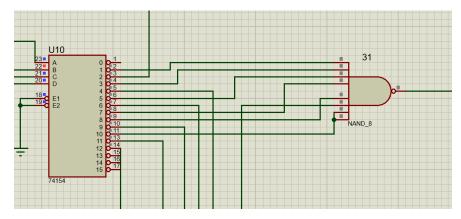This Nand to 31-day months it is connected with (1,3,5,7,8,10,12) if any of them = 0 its output=1




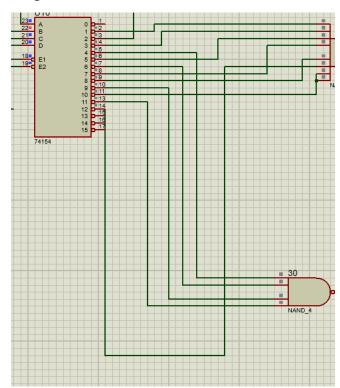This Nand to 30-day months it is connected with (4,6,9,11) if any of them =0 its output=1




3- NOT gate: it is toggle input if input=0 → output=1

It is connected with month 2.

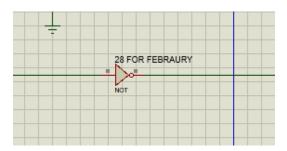

4- AND gates: Its Task to check months and days.

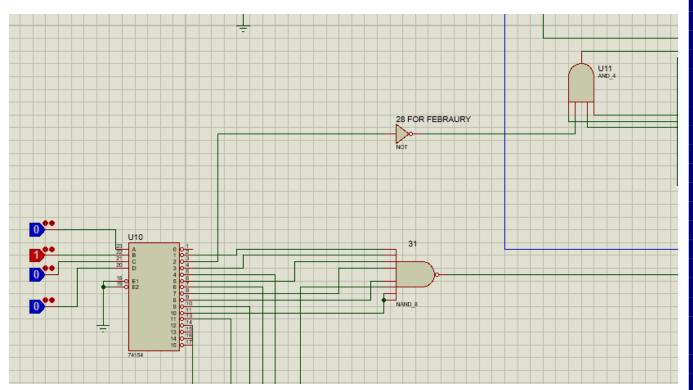For example: if month is 2 and days that display in 7 segment is 28 its output would be 1




And so on with other AND Gates.


5- **OR-3** gates:

If the output from any AND =1 then \rightarrow output=1

3 Input OR Gate

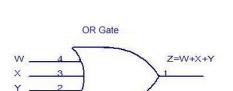

INPUTS		OUTPUT	
W	×	Y	Z
o	0	0	0
0	0	1	*1
0	1	0	1
0	1	1	1
1	O	0	1
1	0	1	1
1	1	0	1
1	1	1	1

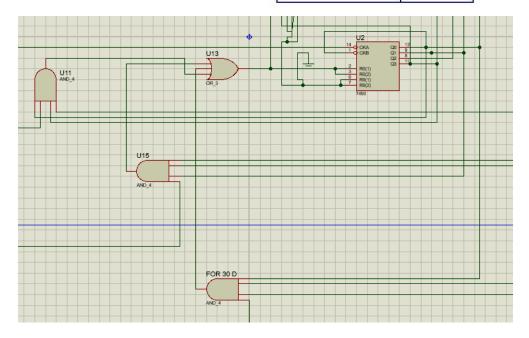

Then output of this OR would rest counters.